

Chapter -3: Current Electricity

- Rate of flow of charges - Current

SI unit : 1 Ampere = 1 coulomb / 1 second

- If the current is not steady, $I = \frac{dQ}{dt}$

- Ohm's Law:

At constant temperature, the potential difference across the ends of wire is directly proportional to the current in the wire

$$V \propto I$$

$$V = IR$$

R = Resistance

$$R = \frac{V}{I}$$

SI unit = Ω

$$1 \Omega = \frac{1V}{1A}$$

Resistance: Opposition offered by the conductor to the flow of current.

Factors affecting Resistance:

$$R \propto l$$

$$R \propto \frac{1}{A}$$

$$R \propto \frac{l}{A}$$

$$R = \frac{\rho l}{A}$$

$\rho \rightarrow$ Resistivity of a specific resistance.

$$\rho = \frac{RA}{l}$$

Resistivity: Resistance offered by a wire of length 1 m and Area of cross section 1 m^2 .

SI unit = $\Omega \text{ m}$.

Conductance: Reciprocal of Resistance

$$G = \frac{1}{R} = \frac{A}{\rho l}$$

SI unit = mho, Ω^{-1} , siemens

Conductivity: Reciprocal of Resistivity

$$\sigma = \frac{1}{\rho} = \frac{l}{RA}$$

SI unit = $\Omega^{-1} \text{ m}^{-1}$, mho m^{-1} , siemens m^{-1} .

Current density: $\vec{J} = \frac{I}{A}$

SI unit = Ampere / m^2

(It is a vector)

Relation between E, σ , J.

$$V = IR$$

$$V = \frac{I \rho l}{A}$$

$$V = J \rho l$$

$$E = J \rho$$

$$E = \frac{J}{\sigma}$$

$$\sigma E = J$$

Drift Velocity: The average velocity of all the electrons after the application of electric field.

- Consider a conductor, N no. of free electrons
- Let $u_1, u_2, u_3, \dots, u_N$ be the initial velocities of all the electrons before applying electric field.
- As the electrons are moving in random possible directions, the average velocity of all the electrons before applying electric field is zero.

$$\frac{u_1 + u_2 + u_3 + \dots + u_N}{N} = 0$$

- Let $v_1, v_2, v_3, \dots, v_N$ be the velocities of electrons after applying electric field
- On applying \vec{E} , e^- are accelerated but immediately in the next collision they lose their acceleration. The velocities of electrons after applying \vec{E} is given as:

$$v_1 = u_1 + a t_1$$

$$v_2 = u_2 + a t_2$$

\vdots

$$v_N = u_N + a t_N$$

adding all equations and dividing by N .

$$\frac{v_1 + v_2 + v_3 + \dots + v_N}{N} = \frac{u_1 + u_2 + u_3 + \dots + u_N}{N}$$

$$+ a \left(\frac{t_1 + t_2 + t_3 + \dots + t_N}{N} \right)$$

$$V_d = 0 + a \tau$$


$$\tau = \frac{t_1 + t_2 + t_3 + \dots + t_N}{N}$$

→ relaxation time : Average time elapsed in between successive collisions

$$\begin{aligned} \vec{F} &= -e\vec{E} \\ ma &= -eE \\ a &= \frac{-eE}{m} \end{aligned}$$

$$\therefore V_d = \frac{-eE\tau}{m}$$

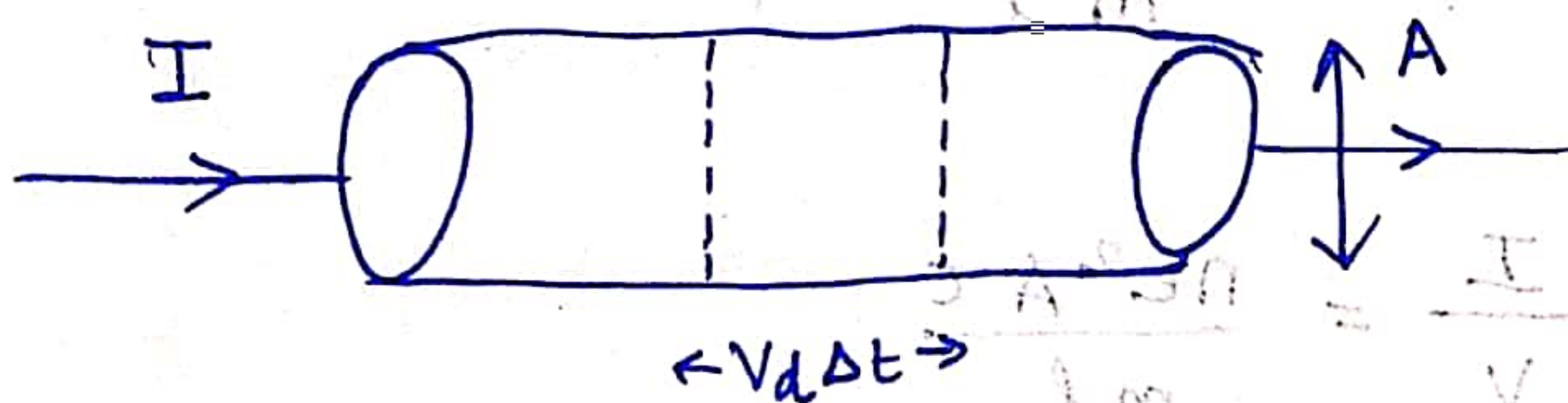Relation between current and drift velocity



A - Area of cross section of the conductor

V_d - Drift velocity of the electrons

Δt - Time interval (For which current is determined)

e - charge of an electron

n - number density of electrons (no. of e^- 's / volume)

Distance moved = $V_d \Delta t$

Volume covered = $A V_d \Delta t$

Total no. of e^- 's moving across this vol } = $n A V_d \Delta t$

Total charge of these e^- 's = $ne A V_d \Delta t$

$$\text{Current} = I = \frac{\Delta Q}{\Delta t} = \frac{ne A V_d \Delta t}{\Delta t} = ne A V_d$$

Ohm's law and Resistivity:

Current through a conductor is given as

$$I = neA V_d$$

$$V_d = \frac{e E \tau}{m}$$

$$I = neA \left(\frac{e E \tau}{m} \right)$$

$$I = \frac{ne^2 A E \tau}{m}$$

$$E = \frac{V}{l}$$

$$I = \frac{ne^2 A V \tau}{m l}$$

$$\frac{I}{V} = \frac{ne^2 A \tau}{m l}$$

$$\frac{V}{I} = \frac{m l}{ne^2 A \tau}$$

$$R = \left(\frac{m}{ne^2 \tau} \right) \frac{l}{A}$$

$$R = \rho \frac{l}{A} \text{ (Comparing with this eq.)}$$

$$\rho = \frac{m}{ne^2 \tau}$$

$$\rho \propto \frac{1}{n} \quad \rho \propto \frac{1}{\tau}$$

Variation of Resistance or resistivity with temperature.

$$R_t = R_0 (1 + \alpha t)$$

$$\rho_t = \rho_0 (1 + \alpha t)$$

$$\alpha = \frac{R_t - R_0}{R_0 t} = \frac{\rho_t - \rho_0}{\rho_0 t}$$

Temp. coefficient of Resistance and Resistivity = α


R_t / ρ_t = Resistance / Resistivity at $t^\circ\text{C}$.

R_0 / ρ_0 = Resistance / Resistivity at 0°C

α = Temp. coefficient Resistance / Resistivity

Temp. difference.

Metals

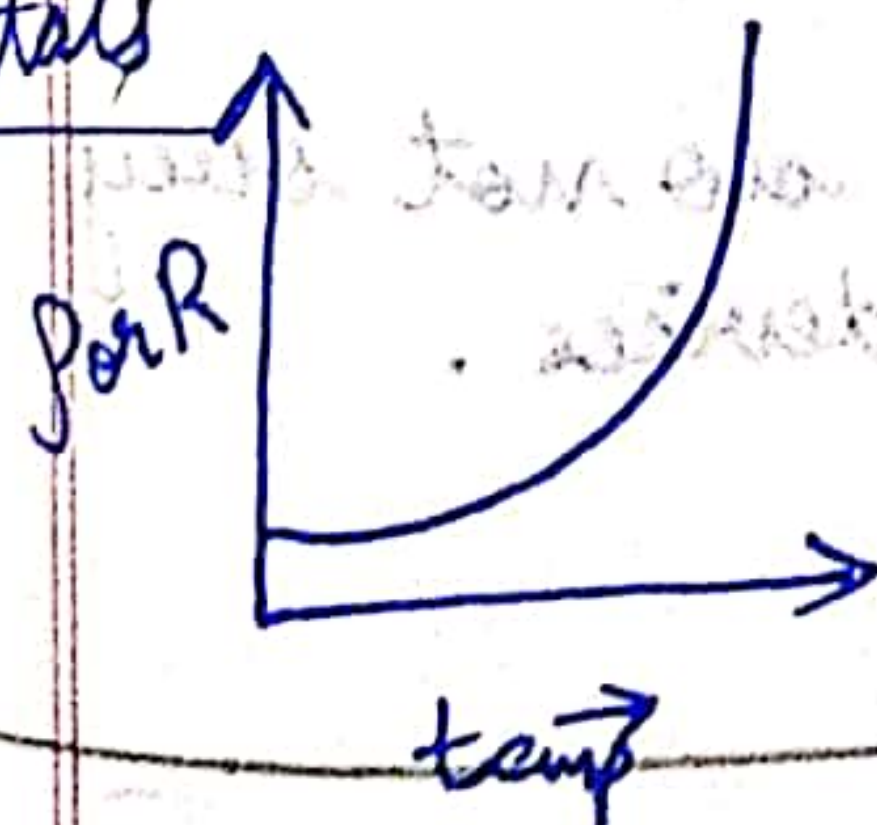


$\alpha = +ve$ and large

As temp. increases, KE increases, frequent collisions occur, τ decrease

$$\rho = \frac{m}{ne^2 \tau}$$


Semi Conductors

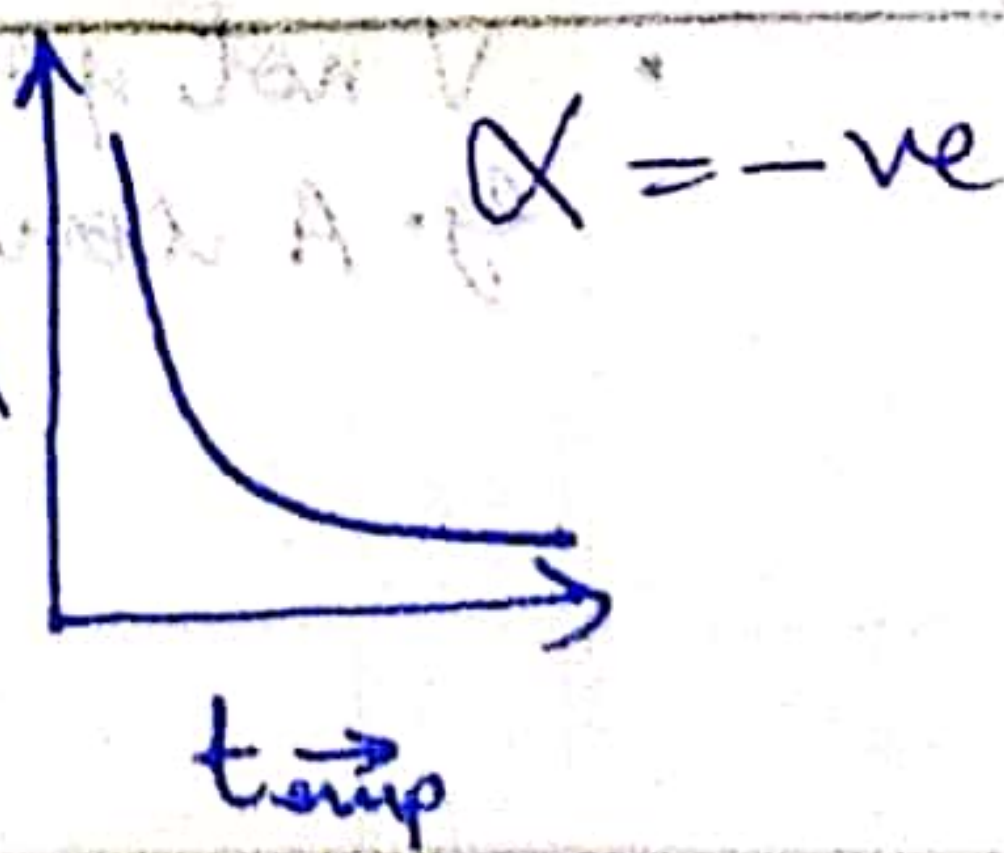As temp increases, no. density of free electrons increase and relaxation time decreases. But increase in 'n' dominates decrease in τ $\therefore R$ decreases with increase in temp.



$\alpha = -ve$

Alloys

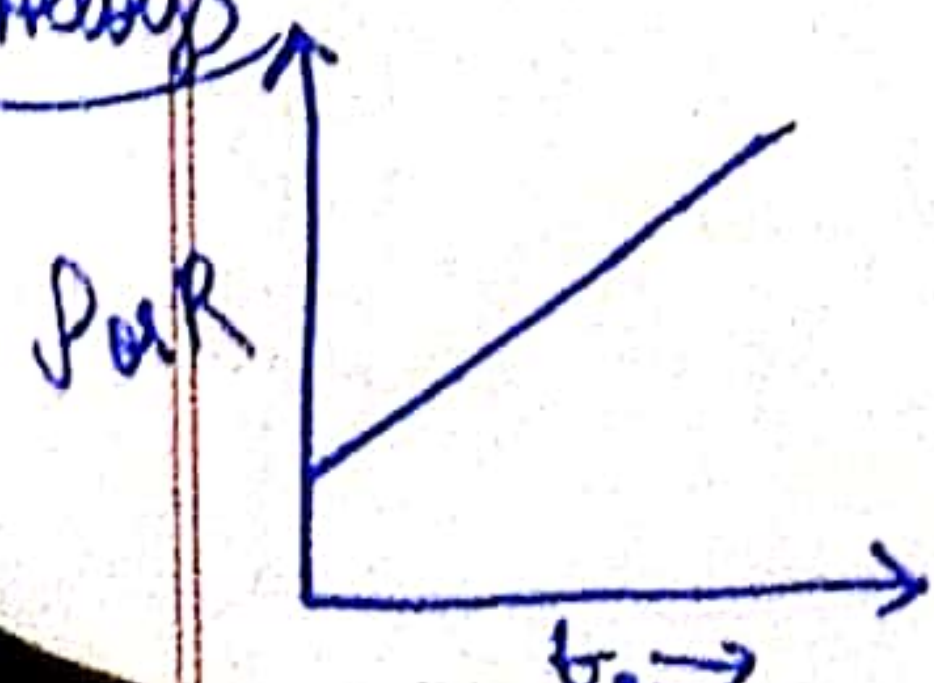


Nichrome, Constantan, Manganin
Alloys show negligible increase in resistance and resistivity with Temp. Hence they are used in standard resistance coil.

As temperature increases

$$G = \frac{Ne^2 \tau}{m}$$

Metals

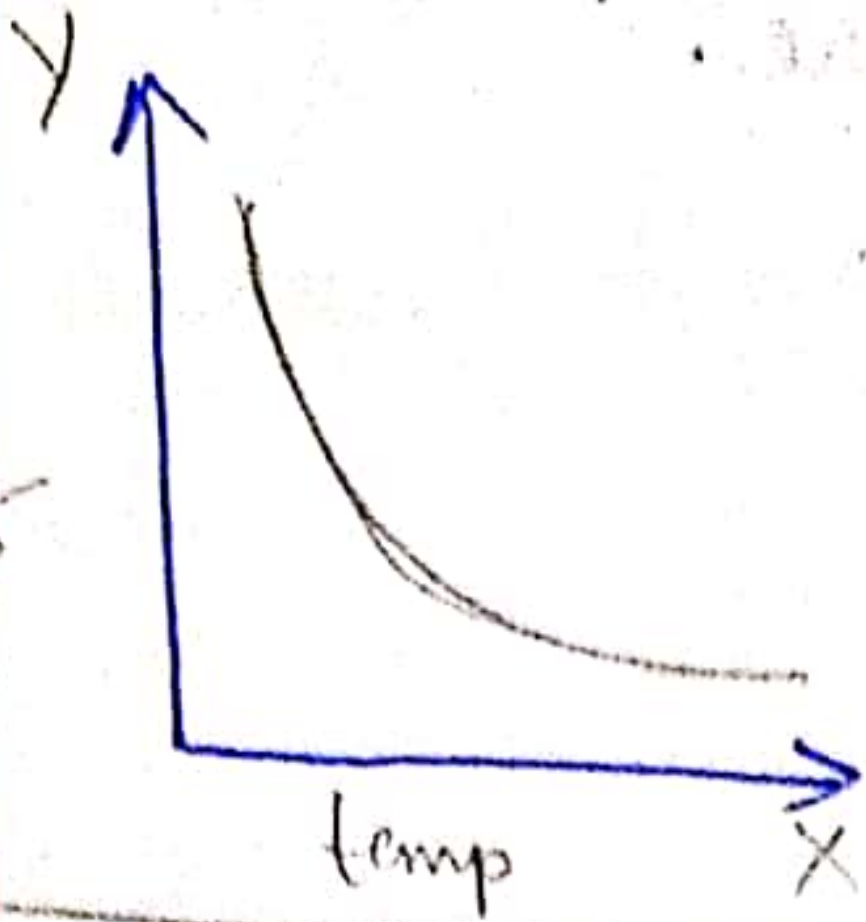


$$R_f = R_0 (1 + \alpha \Delta T)$$

$$R_0 = \frac{R_f}{1 + \alpha \Delta T}$$

Alloys


$$\frac{R_f - R_0}{R_0} = \alpha \Delta T$$
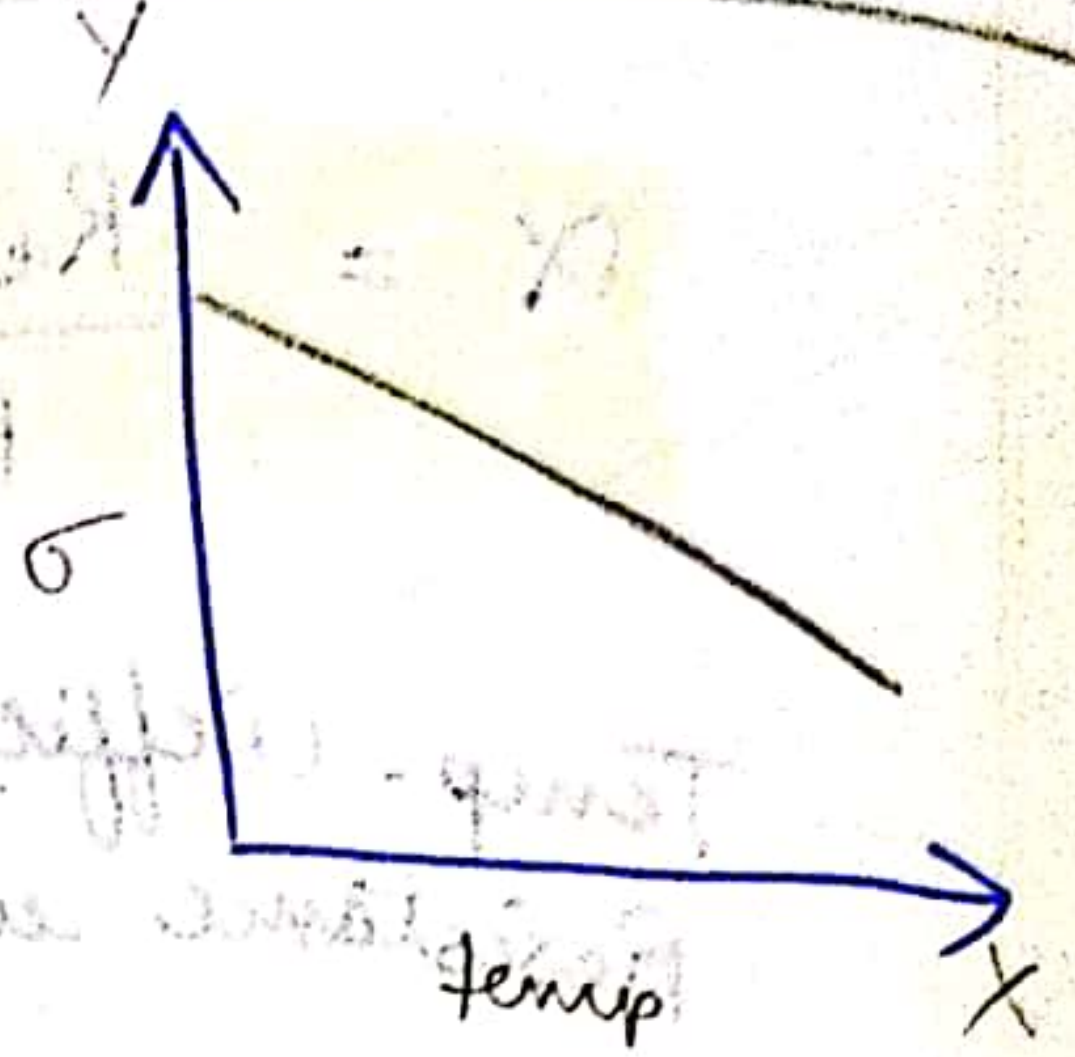
$$\alpha = \frac{R_f - R_0}{R_0 \Delta T}$$



α = coefficient of resistance

Semi conductors

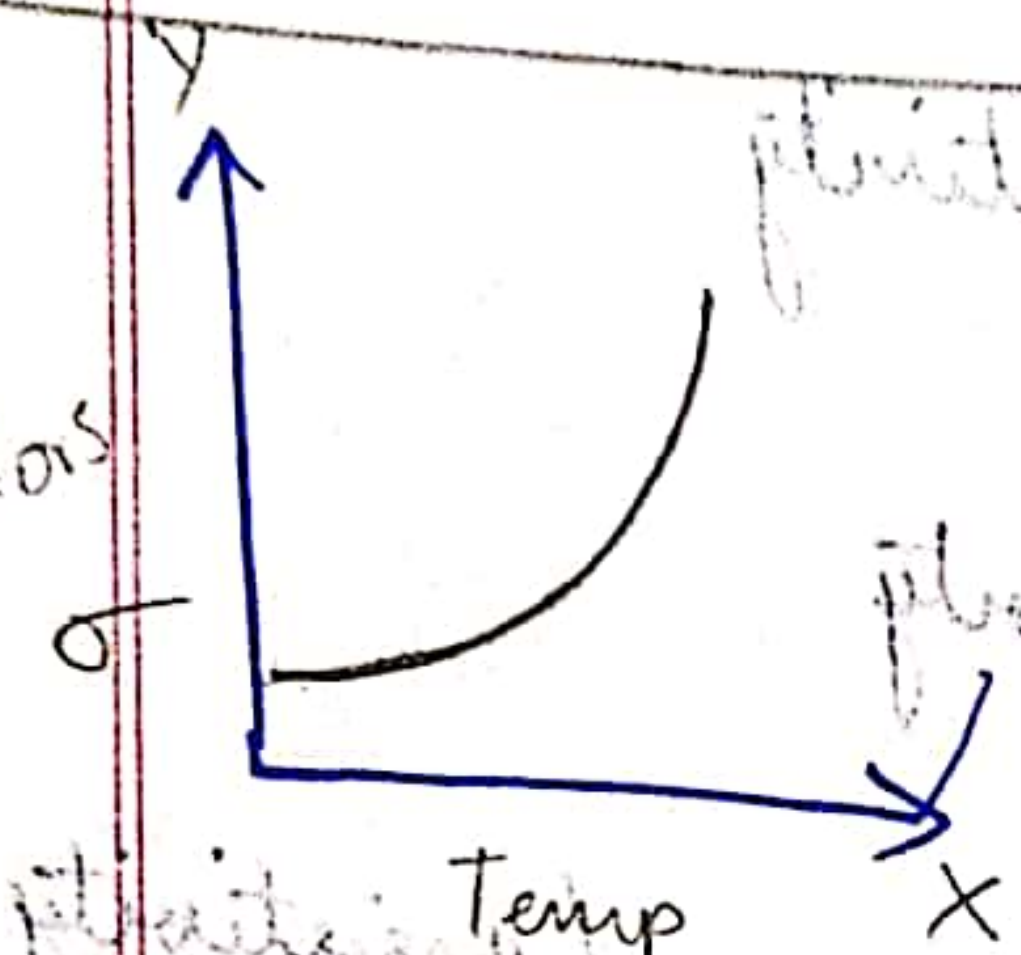

Resistance decreases with temperature

at 0°C to 100°C

Ohmic and non-ohmic devices

Ohmic devices: Devices which obey ohm's law are called ohmic devices.


eg. Metallic conductor at constant temperature

Non ohmic devices: Devices which do not obey ohm's law are called non-ohmic devices.

If it satisfies any one of:


- V not proportional to I: A.

eg. A conductor at high temperature.

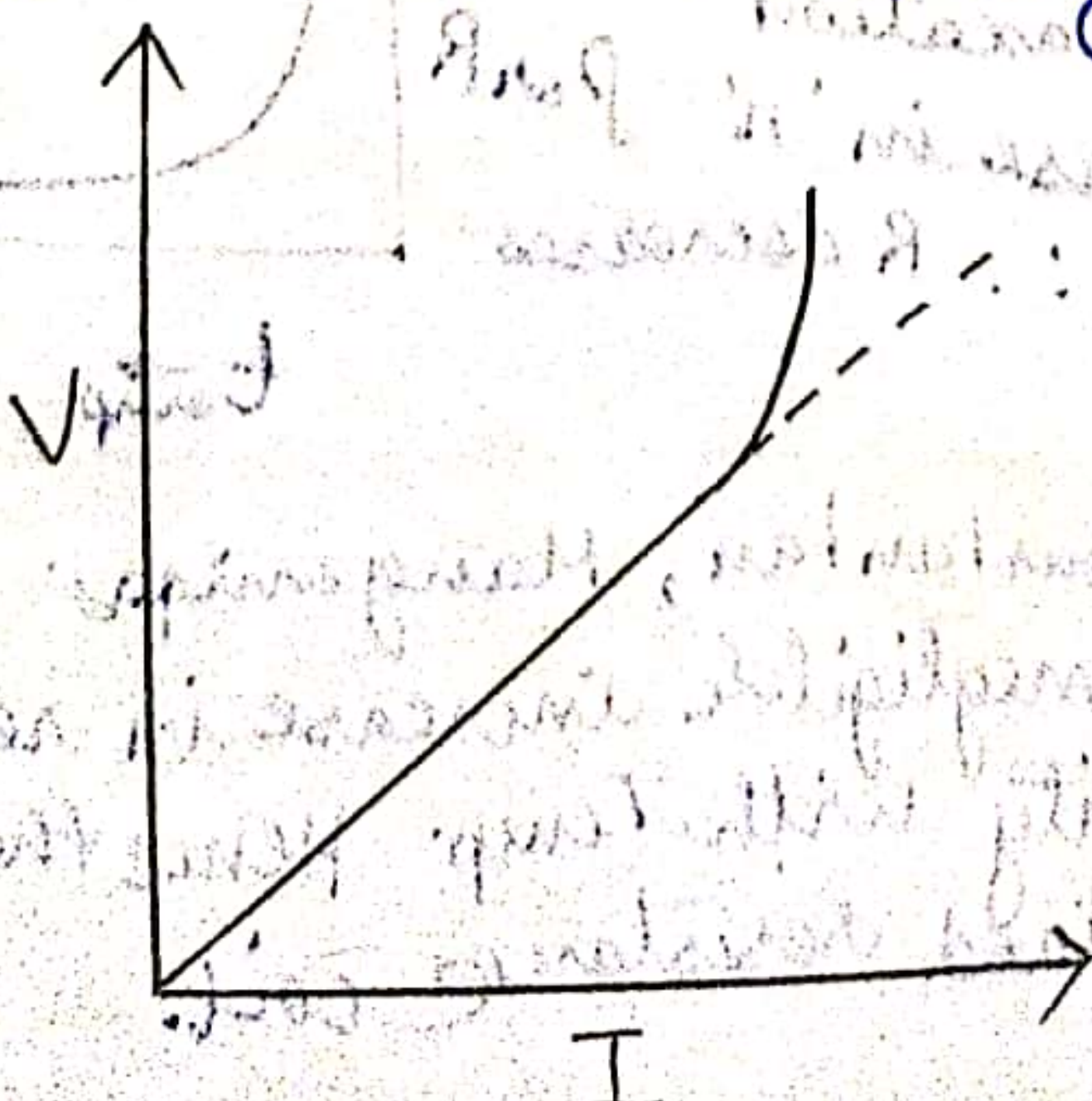


Relation between V and I depends upon the sign of V .

eg: A diode

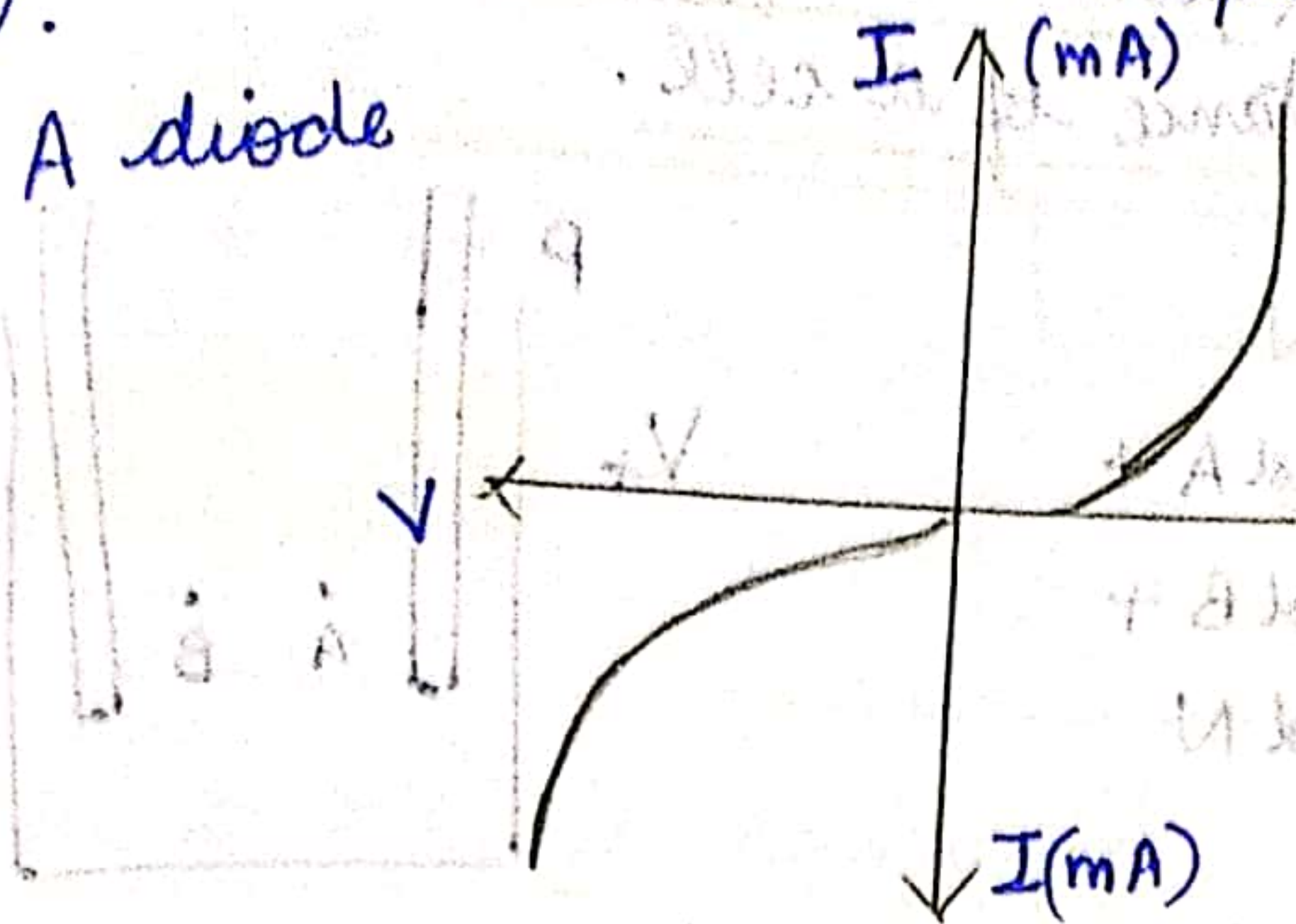

Relation between V and I is not unique. i.e. for a given value of I , there may be more than one value of V .

eg. Gallium Arsenide ($GaAs$)

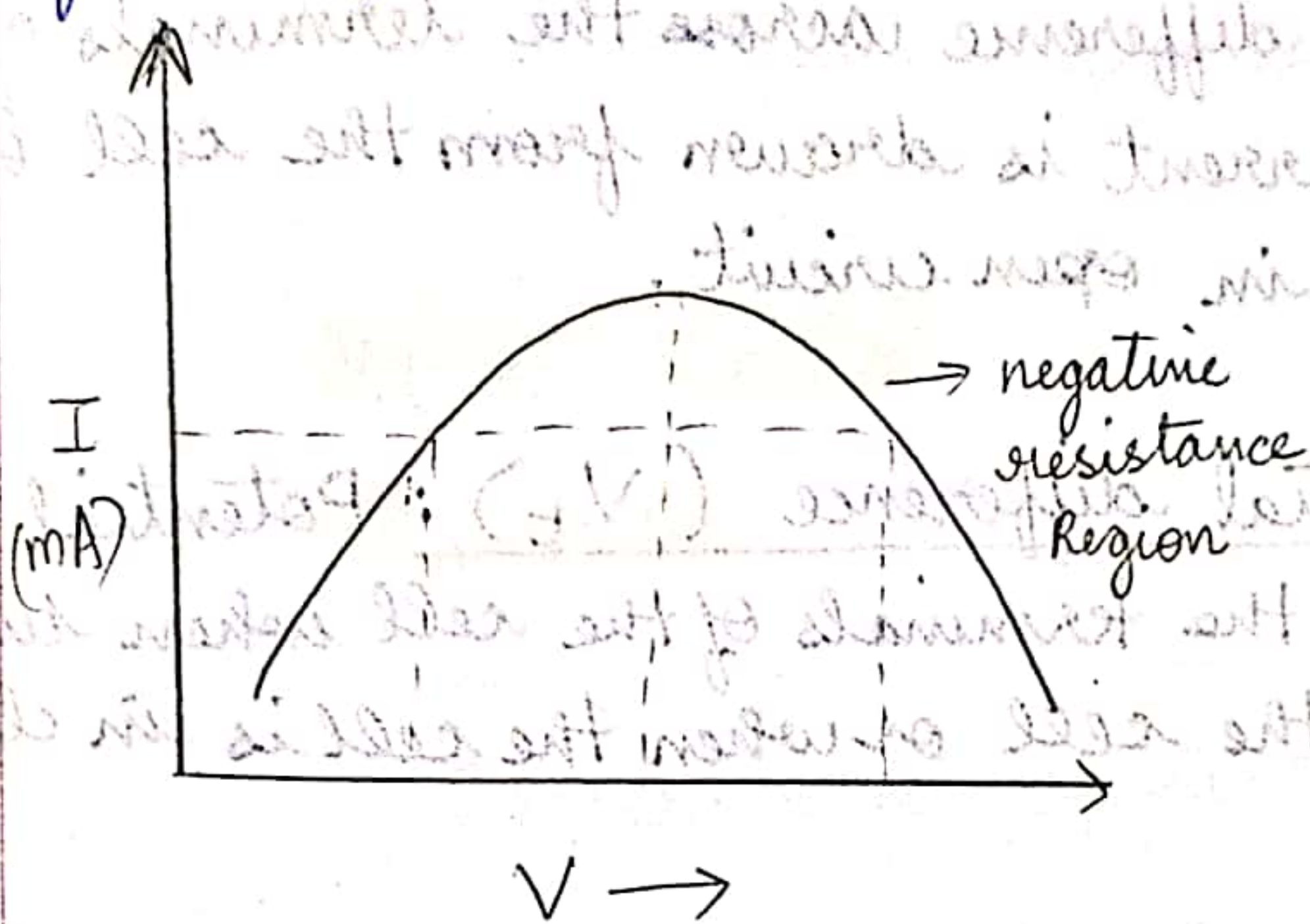

Mobility:

$$\mu = \frac{V_d}{E}$$

Drift Velocity per unit Electric field is called mobility.

$$\mu = \frac{e E \tau}{m E}$$

SI unit = $C \cdot s / kg$

Cm / Vs

$$\mu = \frac{e \tau}{m}$$



EMF, terminal potential difference and internal resistance of a cell.


$$\begin{aligned} & \text{P.d bet P and N} \\ &= \text{P.d bet P and A} + \\ & \quad \text{P.d bet A and B} + \\ & \quad \text{P.d bet B and N} \end{aligned}$$

$$= V_+ + 0 + V_- \quad (Am)I$$

$$= V_+ - V_-$$

→ not a force tho.

= EMF (Electromotive force) of the cell

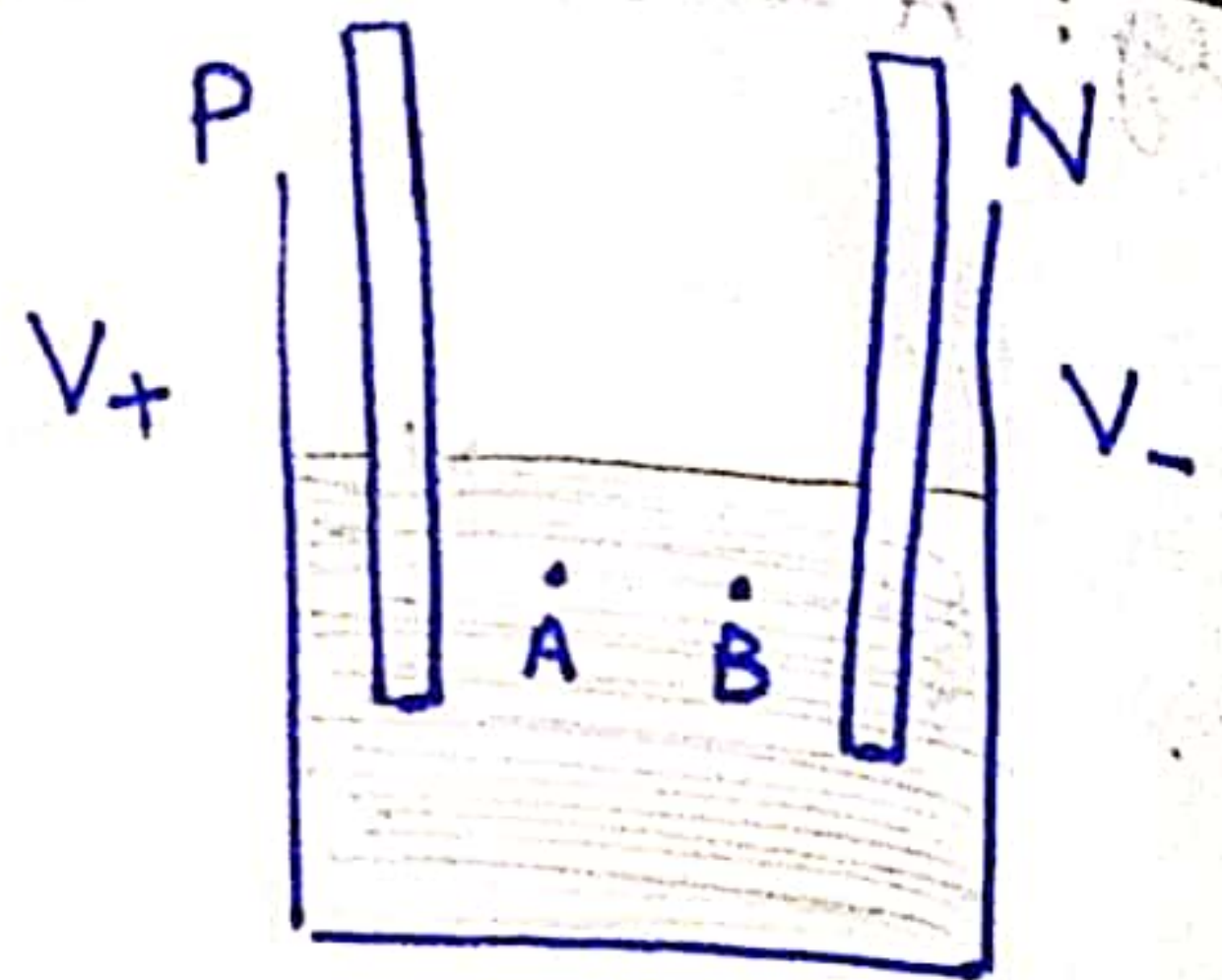

EMF: Potential difference across the terminals of a cell when no current is drawn from the cell or when the cell is in open circuit.

Terminal potential difference (V_t): Potential difference across the terminals of the cell when current is drawn from the cell or when the cell is in closed circuit.

Internal resistance of the cell (r): Opposition offered by the electrolyte of the cell is called internal resistance of the cell. It depends on:

- length of the electrodes
- Nature of the electrolyte
- Concentration of the electrolyte
- Area of cross section of the electrodes
- Temperature.


When current is drawn from a cell:

$$V_t < \mathcal{E}$$

$$I \neq 0, r \neq 0.$$

$$V_t = \mathcal{E}$$

$$I = 0, r = 0.$$

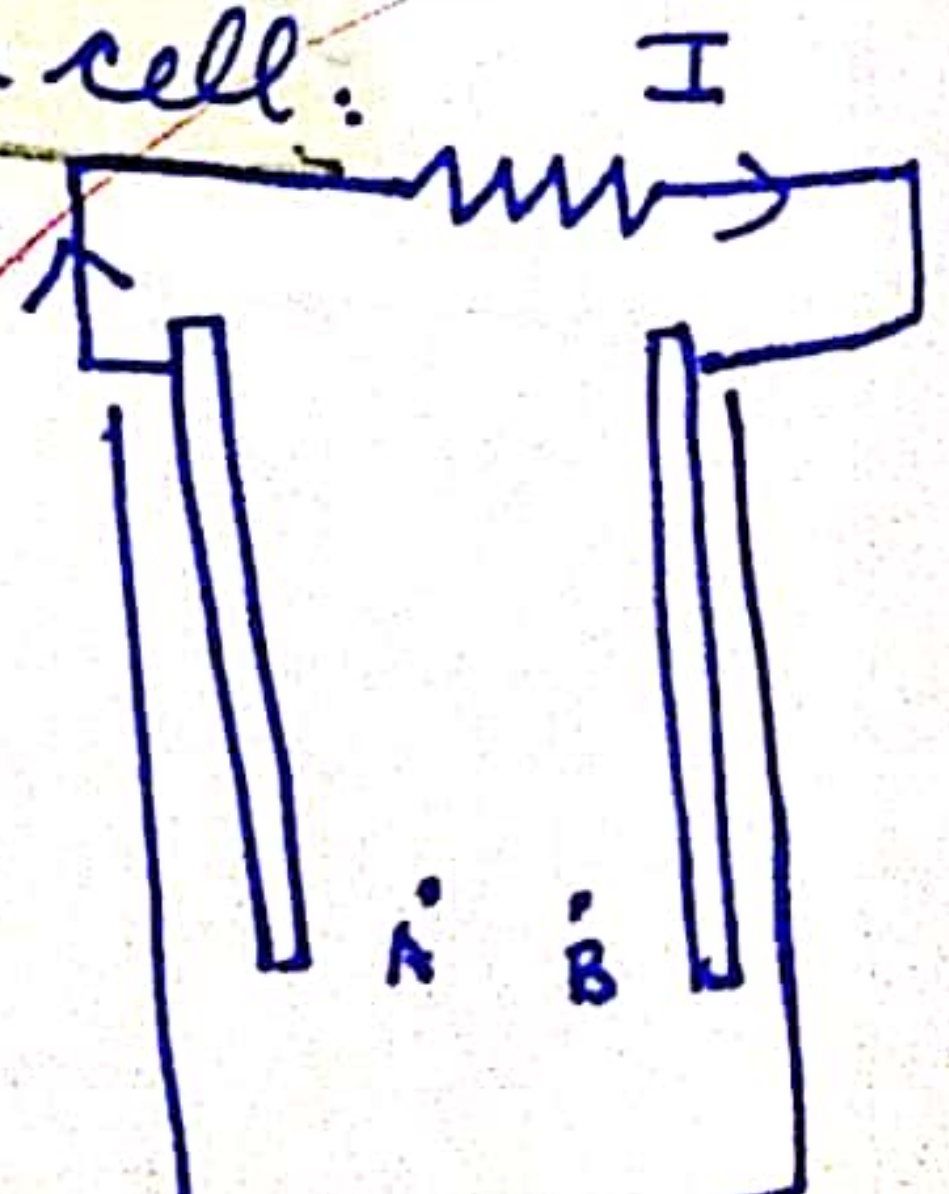


$$V_t = \mathcal{E} - I r$$


$$V_t = I R$$

$$I R = \mathcal{E} - I r$$

$$I = \frac{\mathcal{E}}{R + r}$$

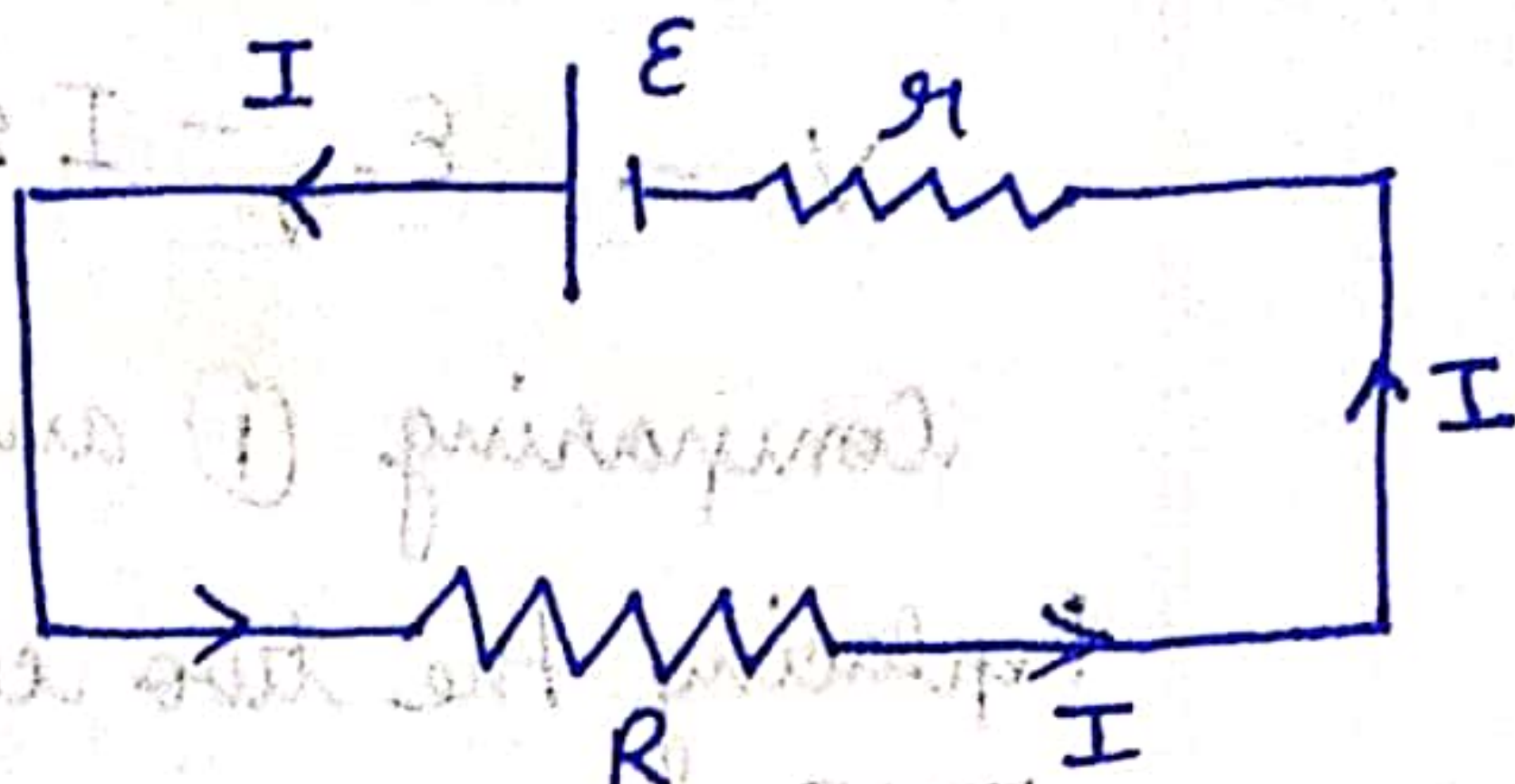

When a cell is recharged


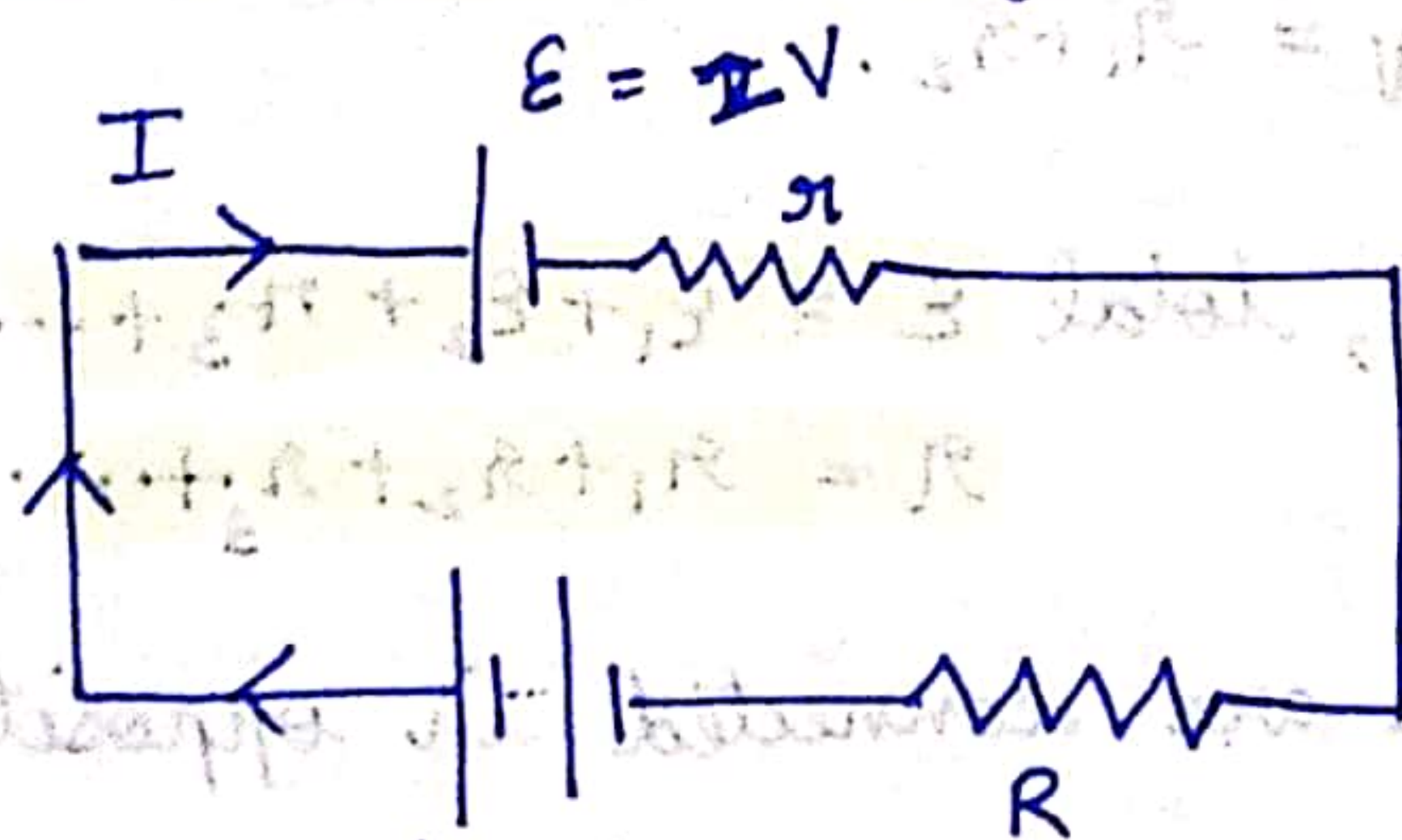


$$V_t = \mathcal{E} + I r$$

$$V_t > \mathcal{E}$$

Combination of Cells

Series combination

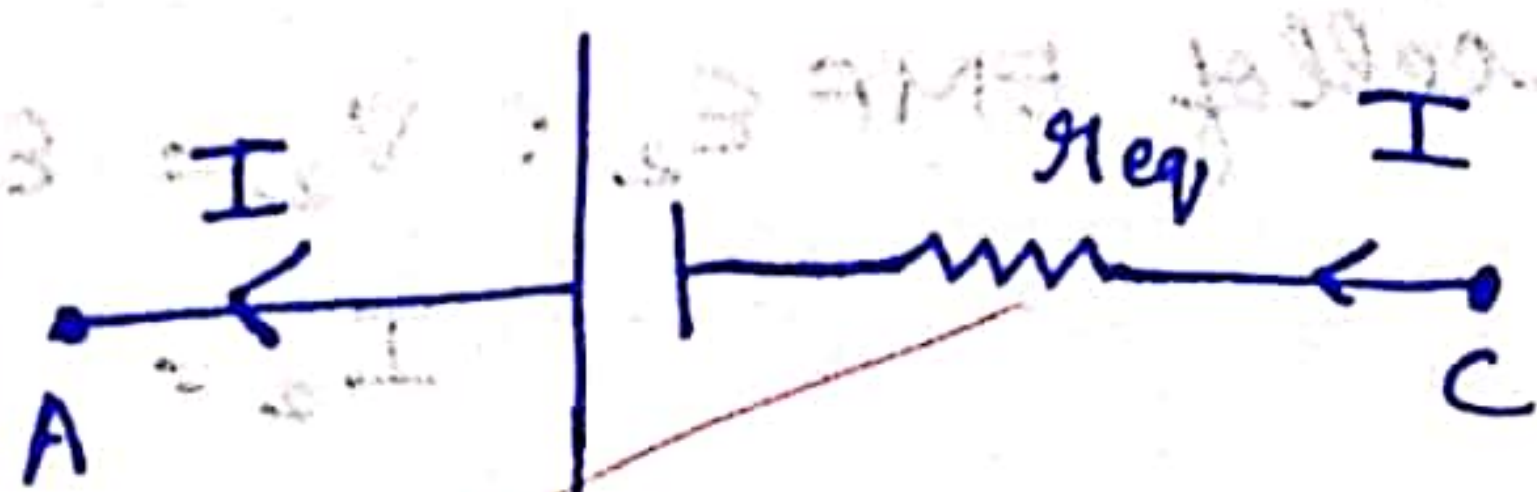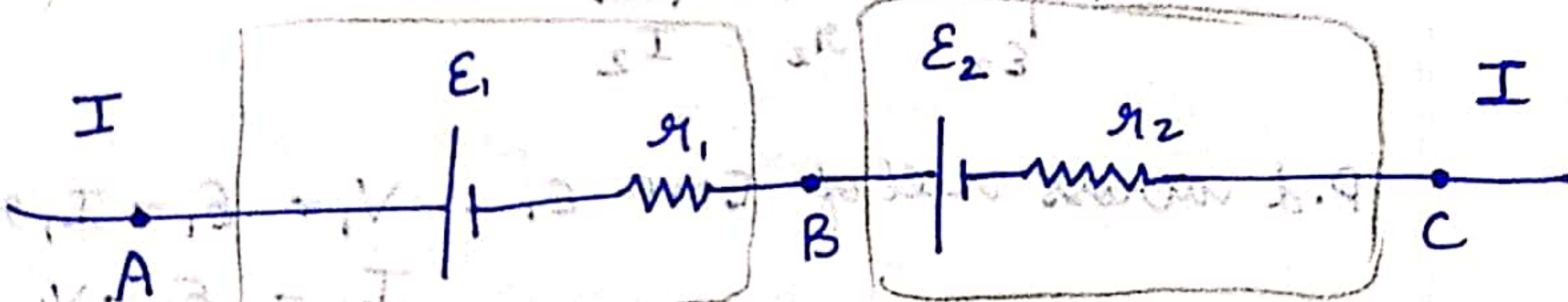

$$\mathcal{E}_{eq}$$

$$V = \mathcal{E} - I r$$

$$V_{AB} = \mathcal{E}_1 - I r_1 \quad V_{BC} = \mathcal{E}_2 - I r_2 \quad V_{AC} = V_{AB} + V_{BC}$$

$$V = \mathcal{E}_1 - I r_1 + \mathcal{E}_2 - I r_2 = (\mathcal{E}_1 + \mathcal{E}_2) - I (r_1 + r_2) \quad \text{--- (1)}$$

$$V = \mathcal{E}_{eq} - I r_{eq} \quad (2)$$

Comparing (1) and (2)

Replacing the two cells with another cell with EMF \mathcal{E}_{eq} and r_{eq} .

$$\therefore \mathcal{E}_{eq} = \mathcal{E}_1 + \mathcal{E}_2$$

$$r_{eq} = r_1 + r_2$$


\therefore In series, total $\mathcal{E} = \mathcal{E}_1 + \mathcal{E}_2 + \mathcal{E}_3 + \dots$

$$r = r_1 + r_2 + r_3 + \dots$$

If the cells are connected in opposition

$$\text{---|H|---} (\mathcal{E}_1 > \mathcal{E}_2) \quad \mathcal{E}_{eq} = \mathcal{E}_1 - \mathcal{E}_2 ; r_{eq} = r_1 + r_2$$

⊗ Parallel Combination:

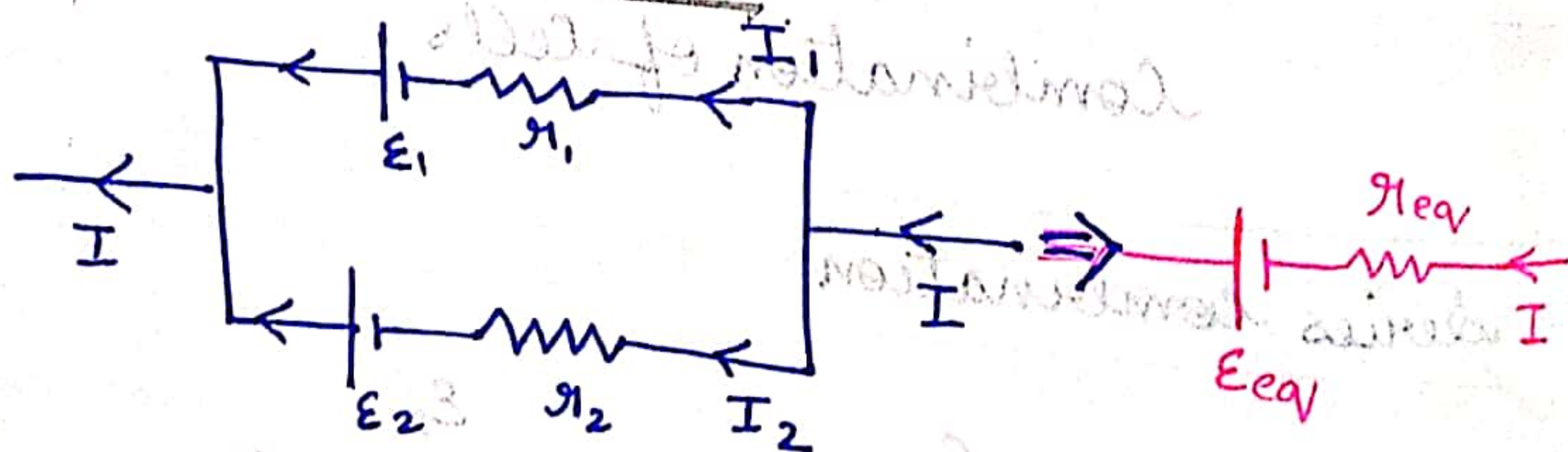

P.d across cell of EMF \mathcal{E}_1 : $V_1 = \mathcal{E}_1 - I_1 r_1$
 $I_1 = \frac{\mathcal{E}_1 - V_1}{r_1} \quad (1)$

P.d across cell of EMF \mathcal{E}_2 : $V_2 = \mathcal{E}_2 - I_2 r_2$
 $I_2 = \frac{\mathcal{E}_2 - V_2}{r_2} \quad (2)$

$V_1 = V_2 = V$ — Parallel combination.

Total $I = I_1 + I_2$

$$I = \frac{\mathcal{E}_1 - V}{r_1} + \frac{\mathcal{E}_2 - V}{r_2}$$

$$= \frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} - V \left[\frac{1}{r_1} + \frac{1}{r_2} \right]$$

$$V \left[\frac{1}{r_1} + \frac{1}{r_2} \right] = \frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} - I$$

$$V \left[\frac{r_2 + r_1}{r_1 r_2} \right] = \frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} - I$$

$$V = \left[\frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} \right] \left[\frac{r_1 r_2}{r_1 + r_2} \right] - I \left[\frac{r_1 r_2}{r_1 + r_2} \right]$$

$$= \left[\frac{\mathcal{E}_1 r_2 + \mathcal{E}_2 r_1}{r_1 r_2} \times \frac{r_1 r_2}{r_1 + r_2} \right] - I \left[\frac{r_1 r_2}{r_1 + r_2} \right]$$

$$= \left[\frac{\mathcal{E}_1 r_2 + \mathcal{E}_2 r_1}{r_1 + r_2} \right] - I \left[\frac{r_1 r_2}{r_1 + r_2} \right] \quad \text{--- (3)}$$

If the 2 cells are replaced by a single cell of EMF \mathcal{E}_{eq} and internal resistance r_{eq} , then

$$V = \mathcal{E}_{eq} - I r_{eq} \quad \text{--- (4)}$$

Comparing (3) and (4)

$$\mathcal{E}_{eq} = \frac{\mathcal{E}_1 r_2 + \mathcal{E}_2 r_1}{r_1 + r_2}$$

$$r_{eq} = \frac{r_1 r_2}{r_2 + r_1}$$

For many no. of cells:

$$\mathcal{E}_{eq} = \frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} + \frac{\mathcal{E}_3}{r_3} + \dots$$

$$\frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} + \dots$$


"n" cells
In parallel, if all have same \mathcal{E} and r ,
 $\mathcal{E}_{eq} = \mathcal{E}$ $r_{eq} = r/n$

In series, if 'n' cells have same \mathcal{E} and r ,
 $\mathcal{E}_{eq} = n\mathcal{E}$ $r_{eq} = nr$

KIRCHHOFF'S RULES

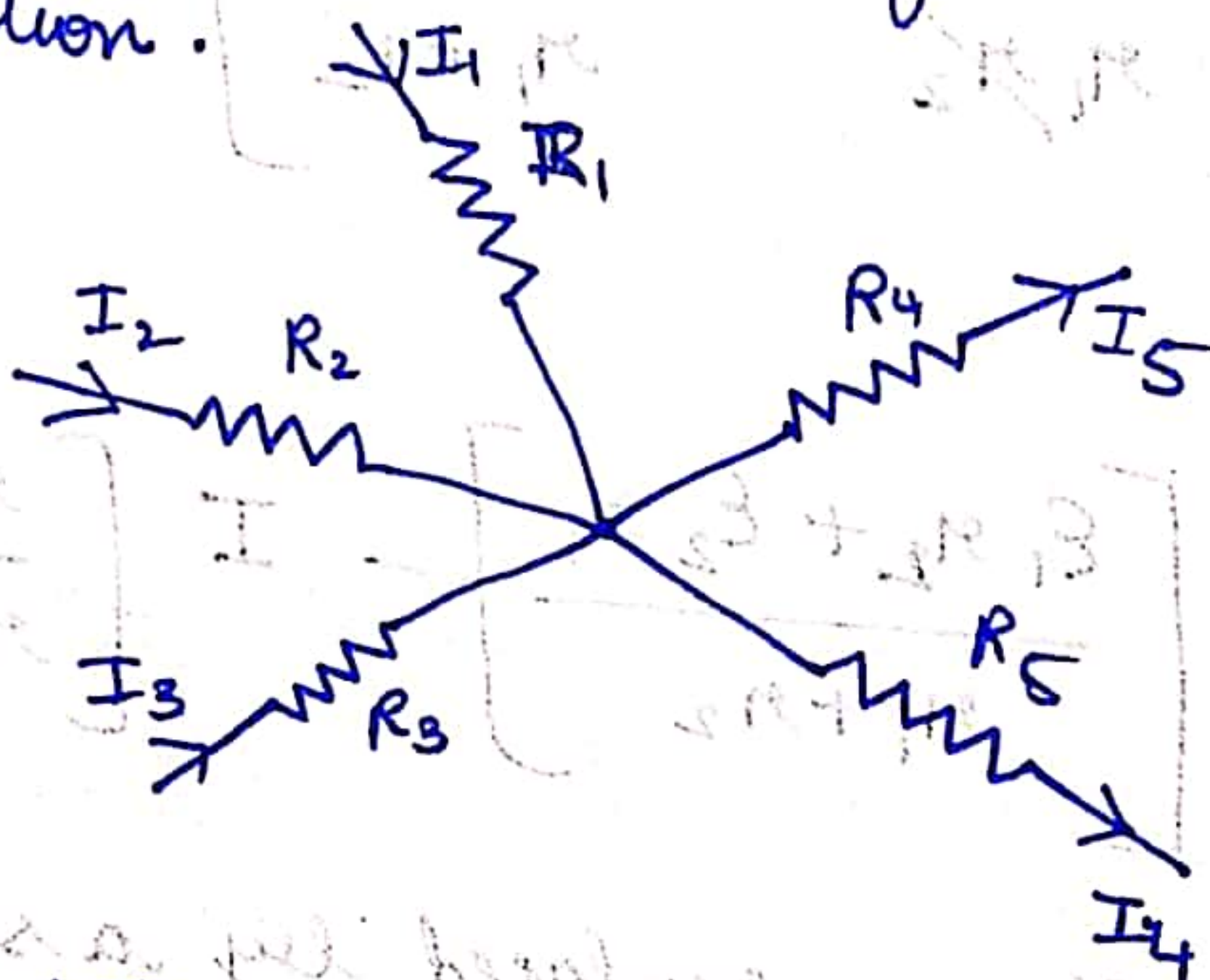a) Junction Rule:


The total sum of current entering the junction is equal to the total sum of current leaving the junction.




$$I_1 + I_2 + I_3 = I_4 + I_5$$

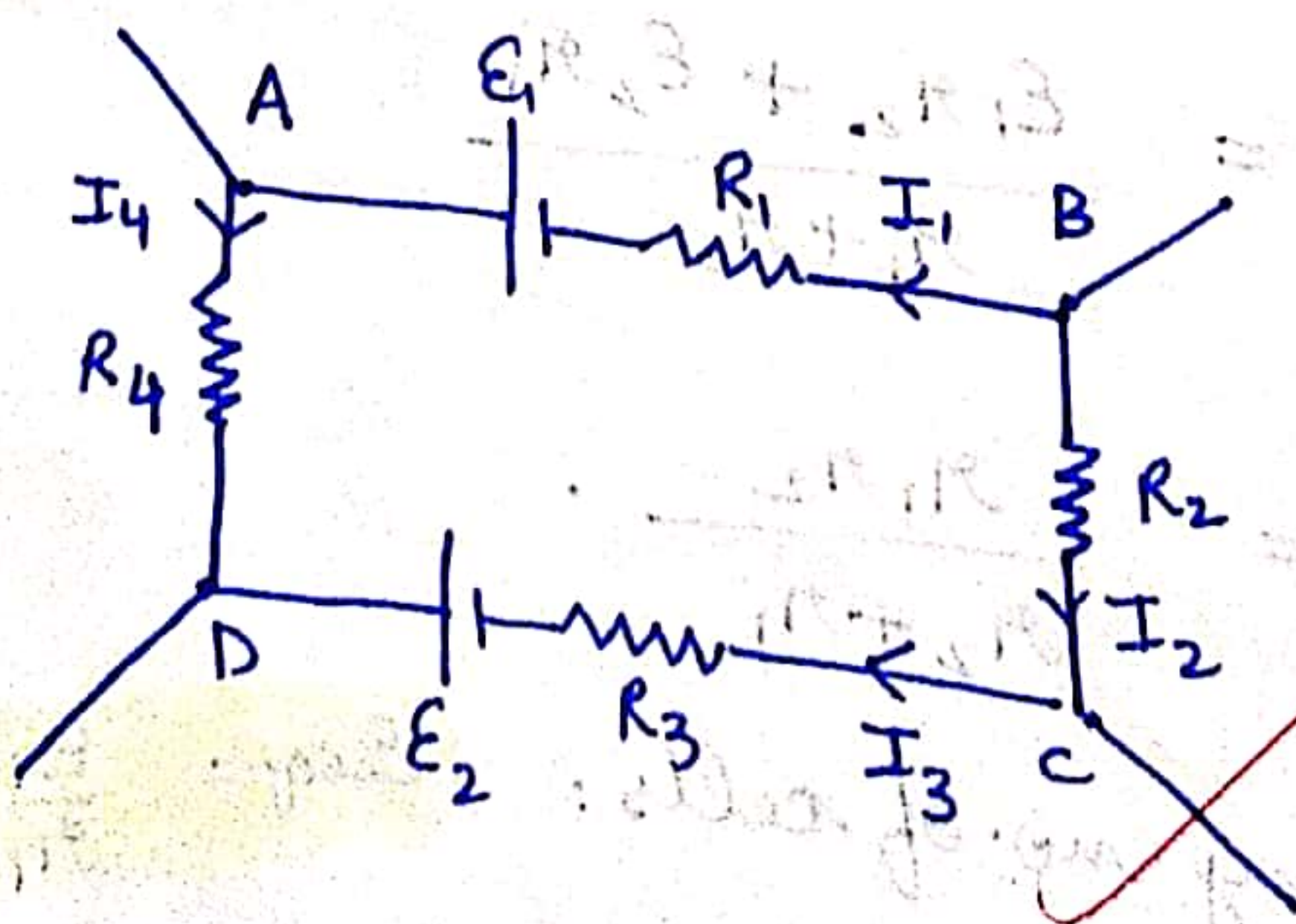b) Loop Rule:

The algebraic sum of potential difference across all the circuit elements in a closed loop is equal to zero.



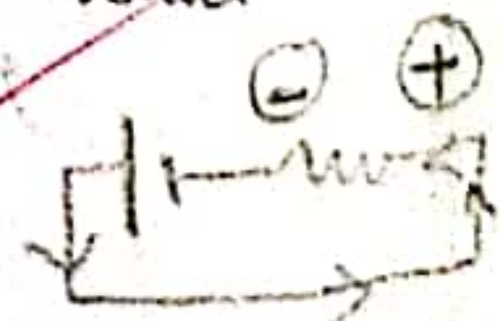
For a resistor, current always flows from high potential to low potential.



$$-\mathcal{E}_1 + I_1 R_1 - I_2 R_2 - I_3 R_3 + \mathcal{E}_2 + I_4 R_4 = 0$$

Application of Kirchhoff's rules

Wheatstone bridge network

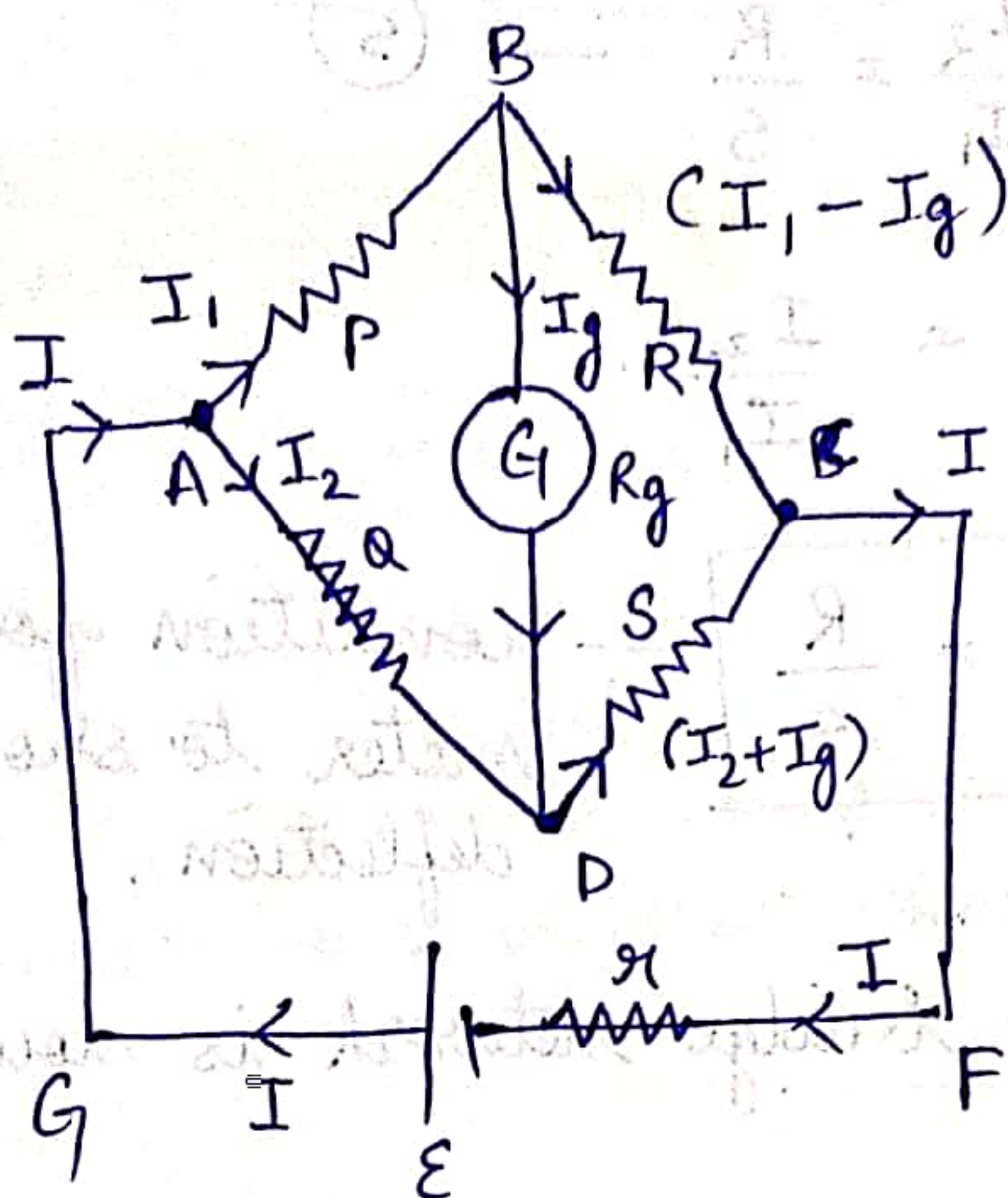

It consists of 4 resistors PQRS connected to a galvanometer and a cell of EMF \mathcal{E} with internal resistance r as shown.

Meter bridge is an example of wheatstone bridge network

Applying junction rule we get $I = I_1 + I_2$ — (1)

Loop ABDA: $-I_1 P - I_g R_g + I_2 Q = 0$ — (2)

Loop BCDB: $-(I_1 - I_g) R + (I_2 + I_g) S + I_g R_g = 0$ — (3)

If the bridge is balanced, the current through the galvanometer is zero.

$\therefore I_g = 0$, equations (2) and (3) becomes:

$$\textcircled{2} \Rightarrow -I_1 P + I_2 Q = 0 \Rightarrow I_2 Q = I_1 P.$$

$$\therefore \frac{I_2}{I_1} = \frac{P}{Q} \text{ — } \textcircled{4}$$

$$(3) \Rightarrow -I_1 R + I_2 S = 0.$$

$$I_1 R = I_2 S.$$

$$\frac{I_2}{I_1} = \frac{R}{S} \quad \text{--- (5)}$$

$$(4) = (5) = \frac{I_2}{I_1}$$

$$\therefore \frac{P}{Q} = \frac{R}{S}$$

condition for galvanometer to show null deflection.

i.e., the bridge network is now balanced.